



THE UNIVERSITY
of ADELAIDE



CRICOS PROVIDER 00123M


School of Computer Science

COMP SCI 2000 / 7081 Computer Systems Lecture 2

adelaide.edu.au

seek LIGHT

The whole system

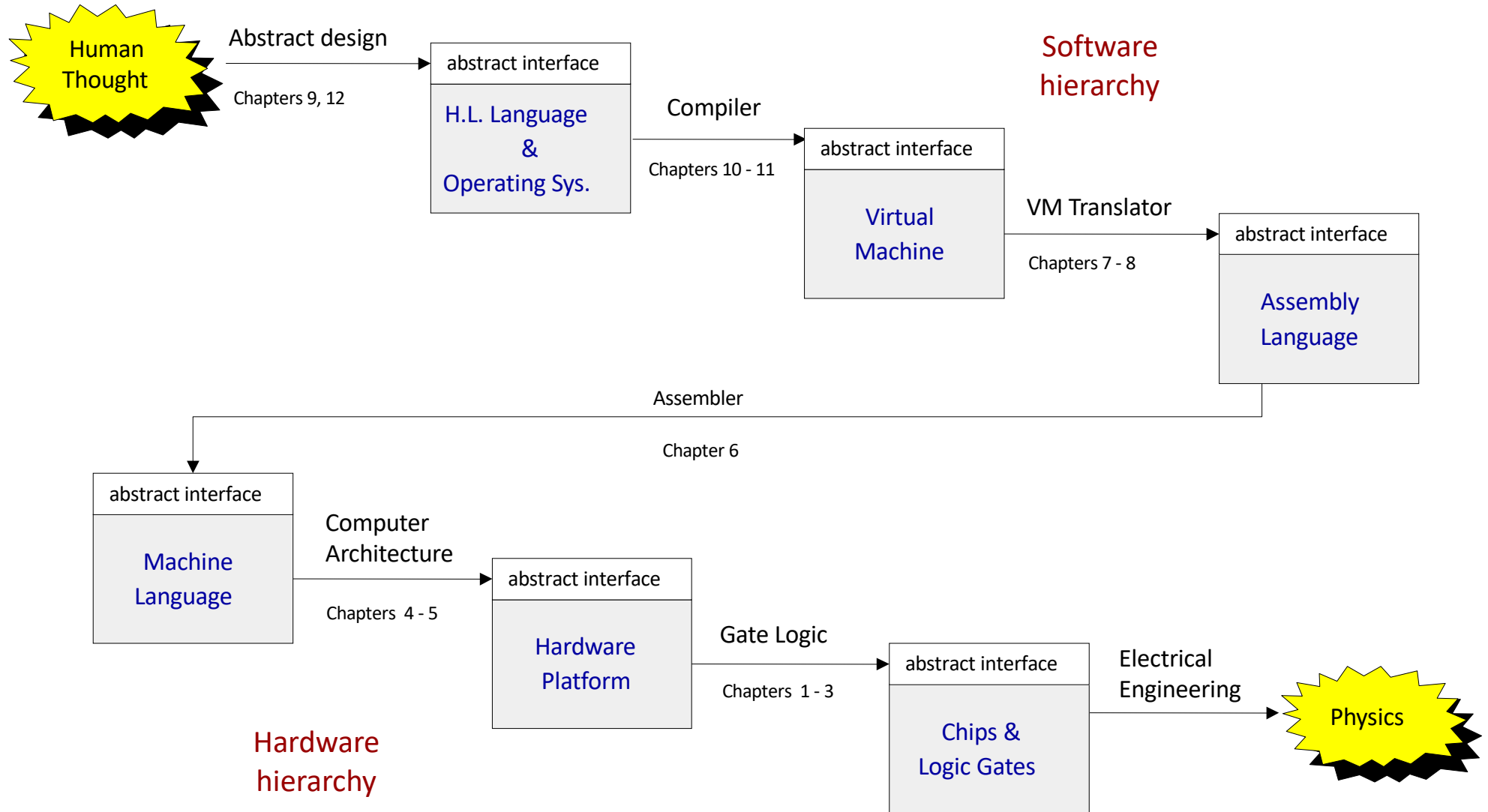


(Abstraction–implementation paradigm)

Review: What is gate logic?

- Our hardware is an inter-connected set of chips.
- Chips are built of simpler chips, down to the simplest structure of all – the elementary logic gate.
- Logic gates are hardware implementations of Boolean functions. This allows us to represent logical statements in computer form.
- Every chip and gate has:
 - An interface: Telling us what it does
 - An implementation: Telling us how it does it
 - Interfaces are a key abstraction mechanism


Review: Example

Interface

 

a	b	out
0	0	0
0	1	1
1	0	1
1	1	0

Implementation

 

All Boolean functions of 2 variables

	Function	x	0	0	1	1
		y	0	1	0	1
Constant 0 = $x \cdot \bar{x}$	Constant 0	0	0	0	0	0
	And	$x \cdot y$	0	0	0	1
	x And Not y	$x \cdot \bar{y}$	0	0	1	0
	x	x	0	0	1	1
	Not x And y	$\bar{x} \cdot y$	0	1	0	0
Add / Difference	y	y	0	1	0	1
	Xor	$x \cdot \bar{y} + \bar{x} \cdot y$	0	1	1	0
	Or	$x + y$	0	1	1	1
	Nor	$\overline{x + y}$	1	0	0	0
	XNor	$x \cdot y + \bar{x} \cdot \bar{y}$	1	0	0	1
x Or Not y	Not y	\bar{y}	1	0	1	0
	If y then x	$x + \bar{y}$	1	0	1	1
Not x Or y	Not x	\bar{x}	1	1	0	0
	If x then y	$\bar{x} + y$	1	1	0	1
Constant 1 = $x + \bar{x}$	Nand	$\overline{x \cdot y}$	1	1	1	0
	Constant 1	1	1	1	1	1

Canonical Form

- We can construct a canonical representation of any boolean function
 - For each row that gives a 1 in its truth table
 - **and** together all terms after applying **not** to any 0 to make it a 1
 - if applied to any other row, the equation will evaluate to 0
 - Then
 - **or** together the equations for every row that gives a 1

- XOR


- $\bar{x}.y + x.\bar{y}$

x	y	x [^] y
0	0	0
0	1	1
1	0	1
1	1	0

- So you only need **and**, **or** and **not** gates

Canonical Form – Mux

a	b	sel	out
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

 

`out = if sel == 0 then a else b`

$$= \bar{a}.b.sel + a.\bar{b}.\bar{sel} + a.b.\bar{sel} + a.b.sel$$

$$= a.\bar{b}.\bar{sel} + a.b.\bar{sel} + a.b.sel + \bar{a}.b.sel$$

$$= a.\bar{sel} + b.sel$$

How to construct **and**, **or** and **not**

- From the truth table:




$$- \bar{x} = \overline{x.x}$$

$$- x.y = \overline{\overline{x.y}}$$

$$- x+y = \overline{\overline{x.y}}$$

x	y	x.y	x+y	\bar{x}	$\overline{x.y}$	$\overline{x.x}$	$\overline{\overline{x.y}}$	$\overline{\overline{x.y}}$
0	0	0	0	1	1	1	0	0
0	1	0	1	1	1	1	0	1
1	0	0	1	0	1	0	0	1
1	1	1	1	0	0	0	1	1

   
- Not(x)
 - Nand(x,x)
- And(x,y)
 - Nand(Nand(x,y),Nand(x,y))
- Or(x,y)
 - Nand(Not(x),Not(y))
- We only need **nand** gates!









Review: Gate logic

- Gate logic – a gate architecture designed to implement a Boolean function

- Elementary gates:

 


- Composite gates:

      

- Important distinction: Interface (*what*) VS implementation (*how*).
-

Example: Building an **And** gate

 

And.cmp

a	b	out
0	0	0
0	1	0
1	0	0
1	1	1

Contract:

When running your **.hdl** on our **.tst**, your **.out** should be the same as our **.cmp**.

And.hdl

```
CHIP And
{
    IN  a, b;
    OUT out;


    PARTS:
        // implementation missing
}
```

And.tst

```
load And.hdl,
output-file And.out,
compare-to And.cmp,
output-list a b out;
set a 0,set b 0,eval,output;
set a 0,set b 1,eval,output;
set a 1,set b 0,eval,output;
set a 1, set b 1, eval, output;
```

Building an **And** gate

 Implementation: $\text{And}(a,b) = \text{Not}(\text{Nand}(a,b))$




And.hdl **And**(a = ?, b = ?, out = ?);

```
CHIP And
{
  IN  a, b;
  OUT out;
  Nand(a = a, b = b, out = x);
  Not(in = x, out = out);
  // Nand(a = x, b = x, out = out);
}
```

Boolean Functions!

 - Each Boolean function has a canonical representation
- The canonical representation is expressed in terms of And, Not, Or
- And, Not, Or can be expressed in terms of Nand alone (or Nor)
- Every Boolean function can be realized by a standard circuit consisting of Nand gates only
- Mass production
- Universal building blocks, unique topology



Number Representation

Decimal	4-bit 2's Complement	Decimal
-8	1000	8
-7	1001	9
-6	1010	10
-5	1011	11
-4	1100	12
-3	1101	13
-2	1110	14
-1	1111	15
0	0000	0
1	0001	1
2	0010	2
3	0011	3
4	0100	4
5	0101	5
6	0110	6
7	0111	7

Binary Addition

Assuming a 4-bit system:

$$\begin{array}{r} \textcolor{red}{0} \text{ } \textcolor{red}{0} \text{ } \textcolor{red}{0} \text{ } \textcolor{red}{1} \\ \hline 0 \ 0 \ 0 \ 1 \\ 0 \ 1 \ 0 \ 1 \\ \hline \textcolor{red}{0} \ 0 \ 1 \ 1 \ 0 \end{array} \quad +$$

No overflow $1 + 5 = 6$

$$\begin{array}{r} \textcolor{red}{1} \text{ } \textcolor{red}{1} \text{ } \textcolor{red}{1} \text{ } \textcolor{red}{1} \\ \hline 1 \ 0 \ 1 \ 1 \\ 0 \ 1 \ 1 \ 1 \\ \hline \textcolor{red}{1} \ 0 \ 0 \ 1 \ 0 \end{array} \quad +$$

Overflow $-5 + 7 = 2$

- Algorithm: exactly the same as in decimal addition
 - Overflow (MSB carry) may need to be dealt with – we usually ignore it.
-

Binary Addition

- How do we know if a 2's complement number is negative?
 - The Most Significant Bit is 1
- There is only one representation of 0
- To negate a number, flip all the bits and add 1
- If you flip all the bits in a number x , you get $-x - 1$
- Sometimes the result of an add operation is wrong!
 - Using subtract to compare numbers needs to account for this effect

$$\begin{array}{r} \textcolor{red}{1} \text{ } 0 \text{ } 1 \text{ } 1 \\ \hline 1 \text{ } 0 \text{ } 1 \text{ } 1 \\ 1 \text{ } 0 \text{ } 1 \text{ } 1 \\ \hline \textcolor{red}{1} \text{ } 0 \text{ } 1 \text{ } 1 \text{ } 0 \end{array} \quad +$$

Bad overflow $-5 + -5 = 6$

$$\begin{array}{r} \textcolor{red}{0} \text{ } 1 \text{ } 0 \text{ } 0 \\ \hline 0 \text{ } 1 \text{ } 0 \text{ } 1 \\ 0 \text{ } 1 \text{ } 0 \text{ } 0 \\ \hline \textcolor{red}{0} \text{ } 1 \text{ } 0 \text{ } 0 \text{ } 1 \end{array} \quad +$$

Bad overflow $5 + 4 = -7$


Building an Adder chip



- Adder: a chip designed to add two integers
 - Proposed implementation:
 - **Half adder**: designed to add 2 bits (we only need one)
 - **Full adder**: designed to add 3 bits (we need $n-1$ of these)
 - **Adder**: designed to add two n -bit numbers.
-

Half adder (designed to add 2 bits)


a	b	sum	carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

 

- A half adder can be built from an **xor** and an **and**
 - the sum column matches xor
 - the carry columns matches and

Full adder (designed to add 3 bits)

a	b	c	sum	carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

 

Implementation: can be based on half-adder gates.

Perspective

- Combinational logic
 - The canonical representation would be too big to use
 - Our adder design is very basic: no parallelism
 - It pays to optimize adders (but we won't do that here)
 - Where is the seat of more advanced maths operations?
a typical hardware/software tradeoff.
-

Summary

- You can construct many gates from NAND – this is just one example of how gates are built up.
- By understanding arithmetic, we can combine gates to add two numbers, then combine full-adders to add larger numbers.